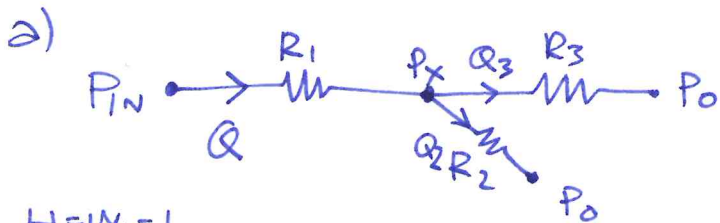


EX. 1



$$V = 1 \mu\text{m/ms}$$



$$Q = V \cdot H \cdot W$$


$$= \frac{1 \mu\text{m} \cdot 30 \mu\text{m} \cdot 30 \mu\text{m}}{1 \text{ms}}$$

$$= 0.9 \cdot 10^{-12} \text{ m}^3/\text{s}$$

$$(54 \text{ nL/min})$$


VERY LOW FLOW RATE!

$$H = W_1 = L$$

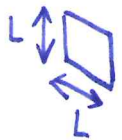

$$R_{eq} = \frac{2 \text{ Area}}{\text{perimeter}} = \frac{2L^2}{4L} = \frac{L}{2} = 15 \mu\text{m}$$

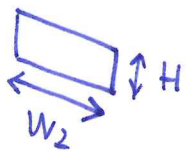
$$R_1 = \frac{8\eta \cdot L_1}{\pi R_{eq}^4} = \frac{8 \cdot 10^{-3} \cdot 1 \text{cm}}{\pi (15 \mu\text{m})^4} = 5 \cdot 10^{14} \left[\frac{\text{Pa} \cdot \text{s}}{\text{m}^3} \right]$$



$$\frac{W_2}{H} > 1.4 \Rightarrow$$

$$R_3 = \frac{12\eta L_3}{(1 - 0.63 \frac{H}{W_2}) H^3 \cdot W_2} = 4.3 \cdot 10^{14} \left[\frac{\text{Pa} \cdot \text{s}}{\text{m}^3} \right]$$
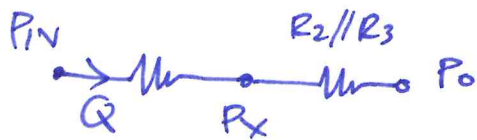
$$R_2 = \frac{R_1}{2} = 2.5 \cdot 10^{14} \left[\frac{\text{Pa} \cdot \text{s}}{\text{m}^3} \right]$$



$$R_2 // R_3 = \frac{2.5 \cdot 4.3}{(2.5 + 4.3)} \cdot 10^{14} = 1.6 \cdot 10^{14}$$

$$P_X = P_0 + R_2 // R_3 \cdot Q = 101 \text{ kPa} + 0.9 \cdot 10^{-12} \frac{\text{m}^3}{\text{s}} \cdot 1.6 \cdot 10^{14} \frac{\text{Pa} \cdot \text{s}}{\text{m}^3} = 101.14 \text{ kPa}$$

144 Pa

$$P_{IN} = P_X + Q \cdot R_1 = 101.14 \text{ kPa} + 0.9 \cdot 10^{-12} \frac{\text{m}^3}{\text{s}} \cdot 5 \cdot 10^{14} = 101.59 \text{ kPa}$$

450 Pa

b) $\eta_{\text{BLOOD}} = 4 \cdot \eta_{\text{WATER}} \rightarrow$



$$R_{TOT} = R_1 + R_2 // R_3$$

$$R|_{\text{BLOOD}} = 4 \cdot R_{TOT} = 4(R_1 + R_2 // R_3)$$

$$P_{IN} = P_0 + Q \cdot 4(R_1 + R_2 // R_3) = 103.37 \text{ kPa}$$

2.37 kPa

(No pressure problems)

$$c) \quad Q_3 = \frac{P_x - P_0}{R_3} = \frac{144 \text{ Pa}}{4.3 \cdot 10^{14} \left[\frac{\text{Pa} \cdot \text{s}}{\text{m}^3} \right]} = 0.33 \cdot 10^{-12} \text{ m}^3/\text{s}$$

$$Q_2 = \frac{P_x - P_0}{R_2} = \frac{144 \text{ Pa}}{2.5 \cdot 10^{14}} = 0.57 \cdot 10^{-12} \text{ m}^3/\text{s}$$

$$(Q_2 + Q_3 = Q = 0.9 \cdot 10^{-12} \text{ OK})$$


Approx: $t_1 = \frac{L_1 \cdot W_1 \cdot H}{Q} = \frac{1 \text{ cm} \cdot 30 \mu\text{m} \cdot 30 \mu\text{m}}{Q} = 10 \text{ sec}$

tot:

$$t_1 + \max(t_2, t_3) \quad t_2 = \frac{0.5 \text{ cm} \cdot 30 \mu\text{m} \cdot 30 \mu\text{m}}{Q_2} = 7.9 \text{ sec}$$

$$t_3 = \frac{4 \text{ cm} \cdot 30 \mu\text{m} \cdot 60 \mu\text{m}}{Q_3} = 218 \text{ sec}$$
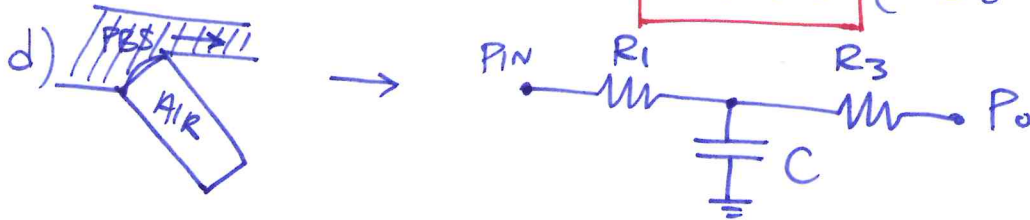
$$t_{\text{tot}} = 10 \text{ sec} + 218 \text{ sec} = \boxed{228 \text{ sec}} \quad (3.8 \text{ minutes})$$



$$\beta = \frac{1}{V_{\text{ol}}} \cdot \frac{\Delta V_{\text{ol}}}{\Delta P} \Rightarrow C = \frac{\Delta V_{\text{ol}}}{\Delta P} = \beta \cdot V_{\text{ol}}$$

$$V_{\text{ol}}(L_2) = L_2 \cdot W_1 \cdot H = 0.5 \text{ cm} \cdot 30 \mu\text{m} \cdot 30 \mu\text{m} = 4.5 \cdot 10^{-12} \text{ m}^3$$

$$C = 7 \cdot 10^{-6} \frac{1}{\text{Pa}} \cdot 4.5 \cdot 10^{-12} \text{ m}^3 = 31.5 \cdot 10^{-18} \frac{\text{m}^3}{\text{Pa}}$$

$$\tau = (R_1 // R_3) \cdot C = \frac{5 \cdot 4.3}{(5 + 4.3)} \cdot 10^{14} \frac{\text{Pa} \cdot \text{s}}{\text{m}^3} \cdot 31.5 \cdot 10^{-18} \frac{\text{m}^3}{\text{Pa}}$$

$$= 2.3 \cdot 10^{14} \cdot 31.5 \cdot 10^{-18} = \boxed{7.2 \text{ ms}}$$

$$e) \quad \eta_{\%} = \frac{Q_3}{Q} = \frac{0.33 \cdot 10^{-12}}{0.9 \cdot 10^{-12}} = \underline{36.6 \%}$$


SOLUTION:

(increase L_2 to increase R_2
and thus reduce Q_2)

low efficiency


↓
need for the actuator

f)

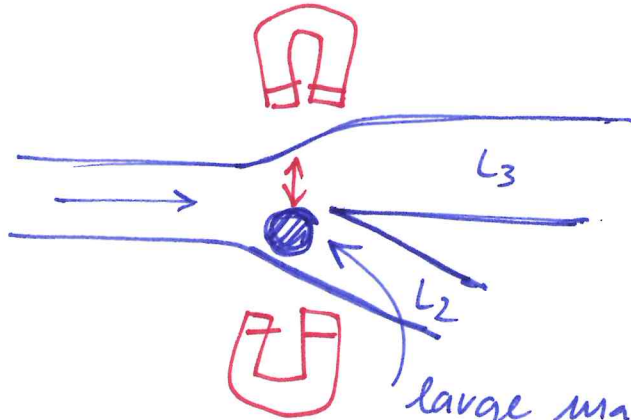

closing L_2 driven by external electromagnet.
large magnetic bead normally



EX. 2

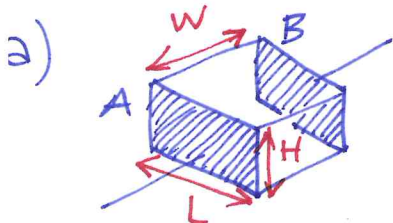

$$R_{SOL} = \rho \cdot \frac{W}{LH} = 0.66 \Omega m \cdot \frac{30 \mu m}{30 \mu m \cdot 60 \mu m} = 11 k\Omega$$



$$C_{SOL} = \epsilon_0 \cdot \epsilon_{FES} \cdot \frac{LH}{W} = \epsilon_0 \cdot 80 \cdot \frac{30 \mu m \cdot 60 \mu m}{30 \mu m} = 42.5 fF$$
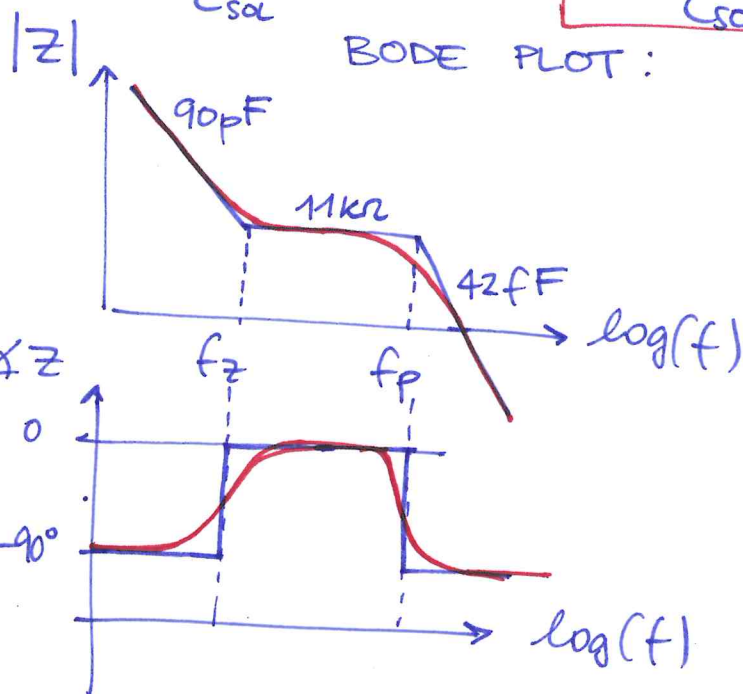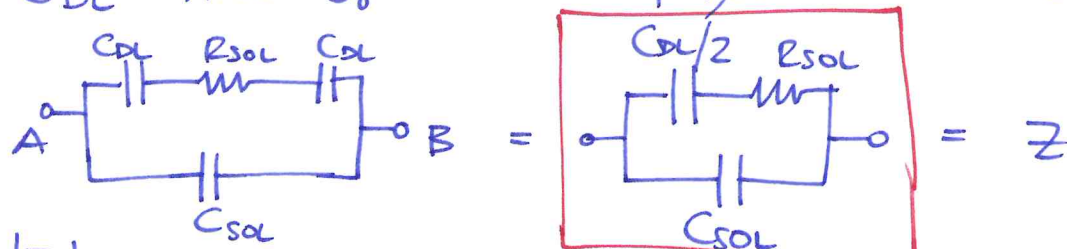
$$C_{DL} = \text{Area} \cdot C_0 = L \cdot H \cdot 0.1 pF/\mu m^2 = 60 \cdot 30 \cdot 0.1 pF = 180 pF$$




$$f_z = \frac{1}{2\pi R_{SOL} \cdot C_{DL}/2} = 160 kHz$$
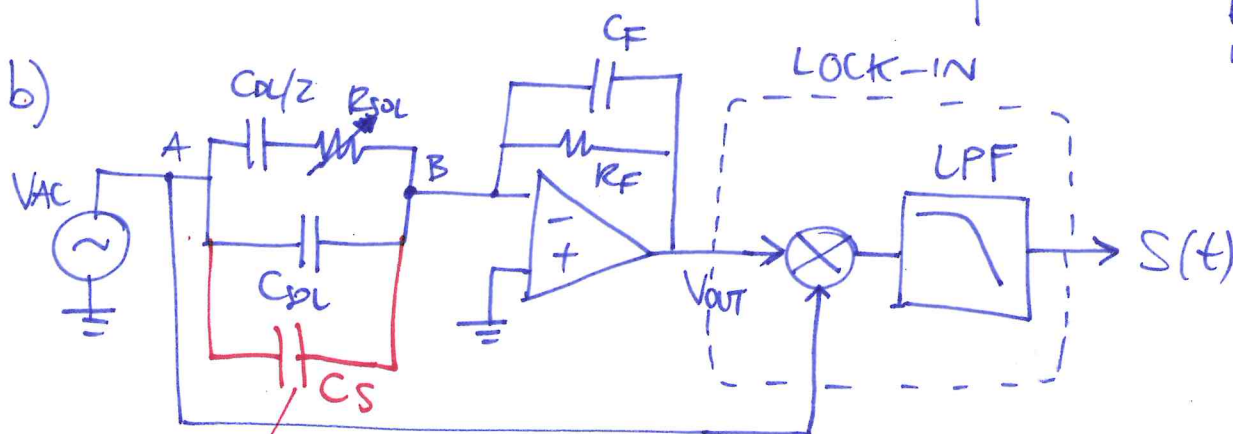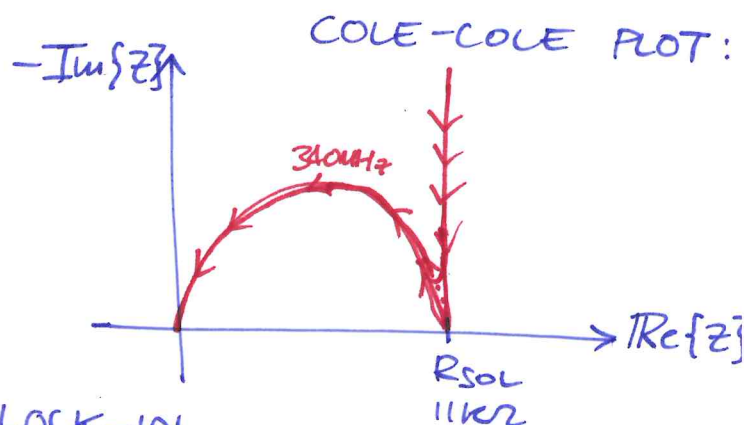
$$f_p = \frac{1}{2\pi R_{SOL} \cdot C_{SOL}} = 340 MHz$$



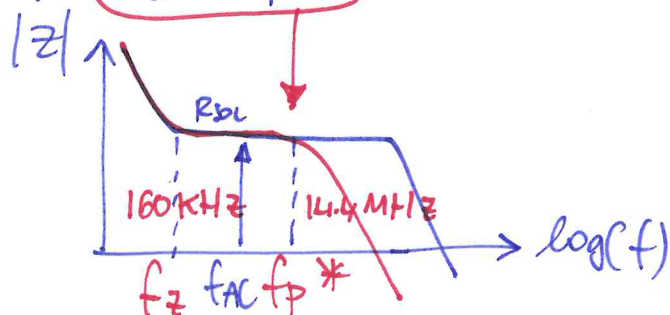
c) $C_S = 1 pF$ → Reduces $f_p^* = \frac{1}{2\pi R_{in} \cdot C_S} = 14.4 MHz$



$$f_z < f_{AC} < f_p^*$$

$$160 kHz < f_{AC} < 14.4 MHz$$

$$f_{AC} = 10 \cdot f_z = 1.6 MHz$$

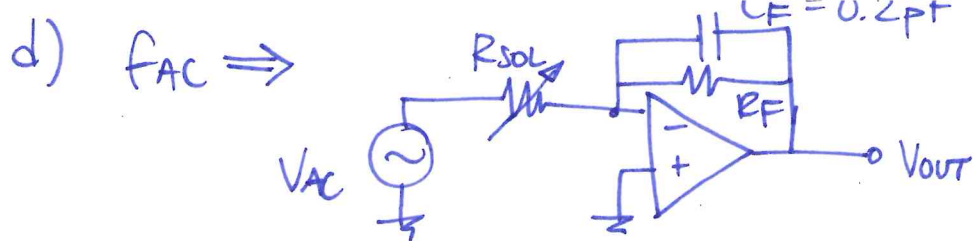

$$V_{OUT} = \frac{V_{AC}}{R_{SOL}} \cdot R_F \Rightarrow V_{OUT}|_{max} = 5V = \frac{0.1V}{11k\Omega} \cdot R_F$$


$$R_F = \frac{5V}{0.1V} \cdot 11k\Omega = \boxed{550k\Omega}$$

full swing (no margin that might be taken...)

CHECK:

$$f_{BW}|_{opamp} \sim \frac{1}{2\pi R_F C_F} = \frac{1}{2\pi \cdot 550k\Omega \cdot 0.2pF} \approx 1.4MHz \sim f_{AC}$$

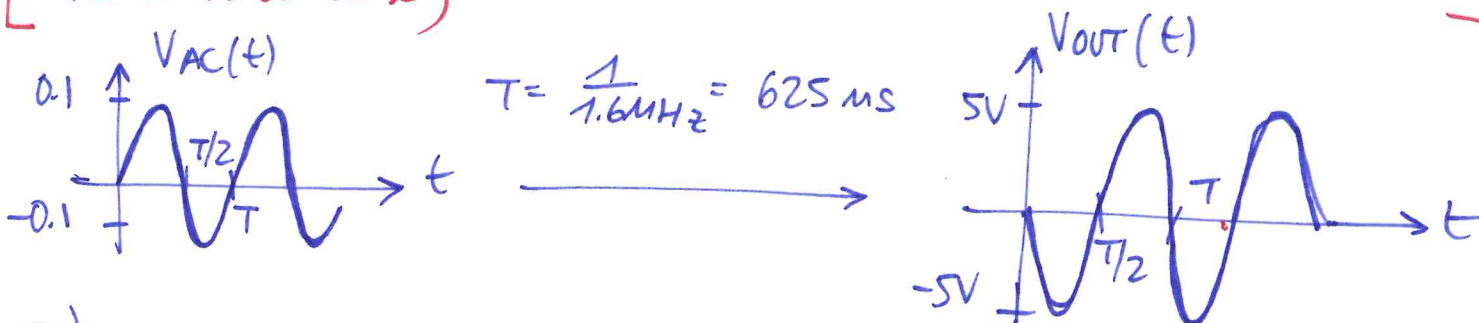(another reason to reduce R_F in a real case) $\leftarrow$ NO GOOD! the pole @ f_{AC}




e)

$$S(t) = - \underbrace{\frac{V_{AC}}{R_{SOL}} \cdot R_F}_{V_{OUT}} \cdot V_{AC} \cdot \sin(2\pi f_{AC} t) \cdot \sin(2\pi f_{AC} t)$$


LPF

$$= - V_{AC}^2 \cdot \frac{R_F}{R_{SOL}} \cdot \frac{1}{2} [\cos(0) - \cos(2\pi \cdot 2 f_{AC} t)]$$
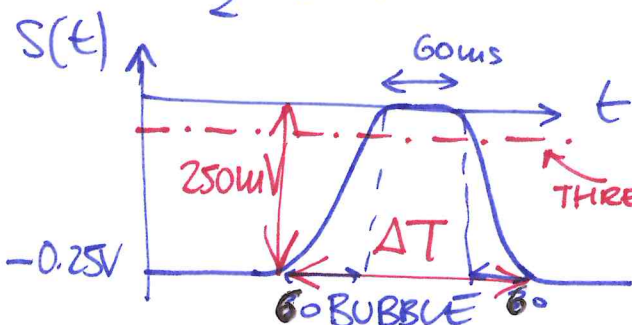
$$= - \frac{1}{2} \cdot (0.1V)^2 \cdot 50 = -0.25V$$



$S=0$ when air fills all the channel

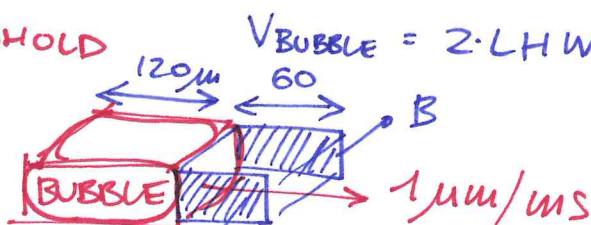


$$\Delta T = \frac{150\mu m}{1\mu m/ms} = 150ms$$

$$BW_{LPF} \sim \boxed{10kHz}$$

$$\tau = \frac{1}{2\pi \cdot 10kHz} = 1.6\mu s$$

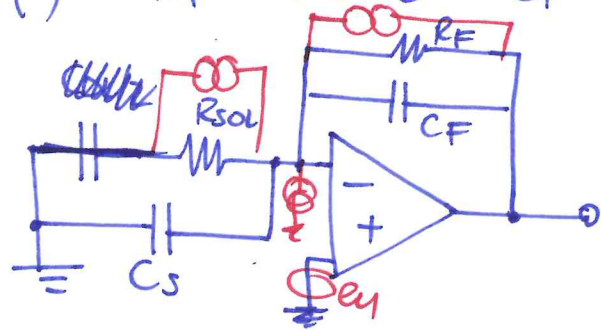f) $R_F = 100 \text{ k}\Omega$ $C_F = 0.5 \text{ pF}$ $C_S = 1 \text{ pF}$



Noise terms:

$$-\sqrt{\frac{4kT}{R_F}} = 0.4 \text{ pA}/\sqrt{\text{Hz}}$$

$$-\sqrt{\frac{4kT}{R_{sol}}} = 1.2 \text{ pA}/\sqrt{\text{Hz}}$$

$$-2\pi f C_{TOT} \cdot e_n$$

$$(C_F + C_S)$$

$$-\frac{e_n}{R_F} = \frac{5 \text{ nV}/\sqrt{\text{Hz}}}{100 \text{ k}\Omega} \text{ negligible}$$

$$-\frac{e_n}{R_{sol}} = \frac{5 \text{ nV}/\sqrt{\text{Hz}}}{11 \text{ k}\Omega} = 0.45 \text{ pA}/\sqrt{\text{Hz}}$$


TOT WHITE TERMS:

$$\sqrt{0.4^2 + 1.2^2 + 0.45^2} = 1.34 \text{ pA}/\sqrt{\text{Hz}}$$

CORNER:

$$2\pi f_c \cdot 1.5 \text{ pF} \cdot 5 \text{ nV}/\sqrt{\text{Hz}} = 1.34 \text{ pA}/\sqrt{\text{Hz}}$$
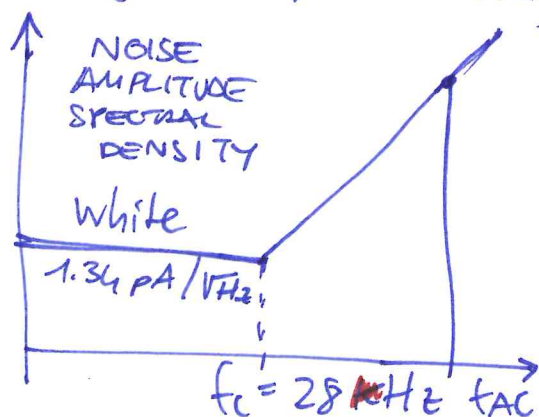
$$f_c = \frac{1.34 \text{ pA}/\sqrt{\text{Hz}}}{(2\pi \cdot 1.5 \text{ pF} \cdot 5 \text{ nV}/\sqrt{\text{Hz}})} = 28.4 \text{ kHz}$$



@ f_{AC} , e_n dominates

(f_{AC} should be reduced!!)

look for:
max SNR(f)...


g) $\sigma_{NOISE} = 20 \text{ ppm}$

$$\Delta Vol|_{min} \cong Vol \cdot 20 \text{ ppm}$$

$$= W \cdot H \cdot L \cdot 20 \text{ ppm} =$$

$$= 60 \cdot 30 \cdot 30 \cdot (\mu\text{m})^3 \cdot 20 \text{ ppm}$$

$$= 1 \mu\text{m}^3$$

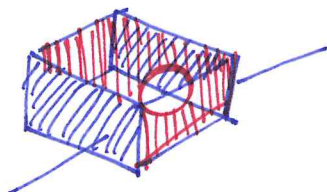

$$\frac{4}{3}\pi r^3 = 1 \mu\text{m}^3 \Rightarrow$$

$$r = 0.62 \mu\text{m} \text{ MIN. DIAMETER}$$

h) YES, it is possible: USING more frequencies to shunt the membrane capacitance.

